

By Craig Anderton From Guitar Player Magazine September 1976

All Capacitors 10v or more All Resistors 1/4 or 1/2 watt 5% tolerance

Drawn by: JD Sleep

Revision: 2003DEC27

Copyright 2003 JD Sleep